

II Semester B.Sc. (I.T.) Examination, June/July 2010
DIGITAL COMPUTER FUNDAMENTALS
(Freshers)

Time : 3 Hours

Max. Marks: 75

Instruction : Answer all questions from Part A, and answer any five from Part B.

PART – A

(10×2+5×1=25)

1. What do you mean by Analog signal ?
2. Represent $275_{(10)}$ in binary.
3. Write the steps to convert decimal fraction to binary.
4. What are floating point numbers ?
5. What are Fundamental gates ?
6. Explain Universal gate.
7. State Demorgan's theorem.
8. What do you mean by don't care condition ?
9. Define Demultiplexer.
10. Write the logic symbol and truth table of Positive and Negative edge triggered J-K flip flops.
11. Briefly explain the following :
 - a) BCD
 - b) ASCII
 - c) Distributive Law
 - d) Encoder
 - e) EPROM.

P.T.O.

PART – B

Answer **any five** questions :

(5×10=50)

1. Perform the following :

i) $10011_{(2)} = ?_{10} = ?_8$

ii) $CA02_{(16)} + FCA_{(16)} = ?$

iii) $275_{(8)} = ?_{10} = ?_{16}$

iv) $160_{(10)} = ?_{(BCD)}$

v) $16.75_{(10)} = ?_{(2)}$

2. What do you mean by Combinational Logic Circuits ? Where they are used ?

3. What is a gate ? How can we convert NAND gate to AND, OR and NOT gate ?

4. Write the steps to simplify given SOP expression using K-MAP with an example.

5. Explain the applications of multiplexer.

6. What are the various Combinational Function Devices ?

7. How can a JK Flip Flop be converted to a D Flip Flop and T Flip Flop ?

8. Explain the difference between Static and Dynamic RAM.
