

I Semester B.Sc. (I.T.) Examination, June/July 2010
INTRODUCTION TO DIGITAL ELECTRONICS

Time : 3 Hours

Max. Marks : 75

PART – A

Answer **all** questions :

(10×2+5×1=25)

1. What is Gate ? Mention the different types of gates.
2. Why Boolean Algebra is needed for the computer system ?
3. Construct an AND gates using NAND gates.
4. What is the significance of using De Morgan's Theorems ?
5. Write any two applications of Flip-Flops.
6. Define Synchronous Counters.
7. Differentiate between Diodes and Transistors.
8. What do you mean by Digital Amplification ?
9. What is Amplifier ?
10. Define the concept of Sampling Rate.
11. Explain the following terms :
 - a) Boolean Algebra
 - b) Commutative laws
 - c) Truth table
 - d) Timing Diagrams
 - e) Multiplexers.

P.T.O.

PART – B

Answer **any five** of the following questions :

(5×10=50)

1. Explain the three Boolean operators with an examples.
 2. State and prove De-Morgan's theorem.
 3. Explain De multiplexers with neat block and circuit diagrams of a 1- of–4 Demultiflexers.
 4. Discuss the specification for the four bit binary adder.
 5. Explain the Bipolar junction transistors.
 6. How can you achieve amplification using a BJT ?
 7. Explain the functioning of a FET and give out some digital application of FET.
 8. Explain the characteristics of an OP-Amp.
-